

Sol

$$x = c_1 e^t + c_2 e^{-t} - 1$$

$$y = c_1 e^t - c_2 e^{-t} - 1.$$

) $\frac{dx}{dt} = 2y - 1, \quad \frac{dy}{dt} = 1 + 2x$

Sol

$$x(t) = c_1 e^{2t} + c_2 e^{-2t} - \frac{1}{2}$$

$$y(t) = c_1 e^{2t} - c_2 e^{-2t} + \frac{1}{2}$$

RLC-Circuit

An RLC-series circuit consists of a resistor, a conductor, a capacitor and an emf as shown in the figure.

Using the Kirchhoff's law

i.e. sum of the voltage drops across the three elements inductor, resistor


and capacitance equal to the external source

E. Thus the RLC-circuit is modeled by

$$L \frac{dI}{dt} + RI + \frac{1}{C} Q = E(t) \quad \text{--- (1)}$$

which contains two independent Q and I

Since $I = \frac{dQ}{dt}$

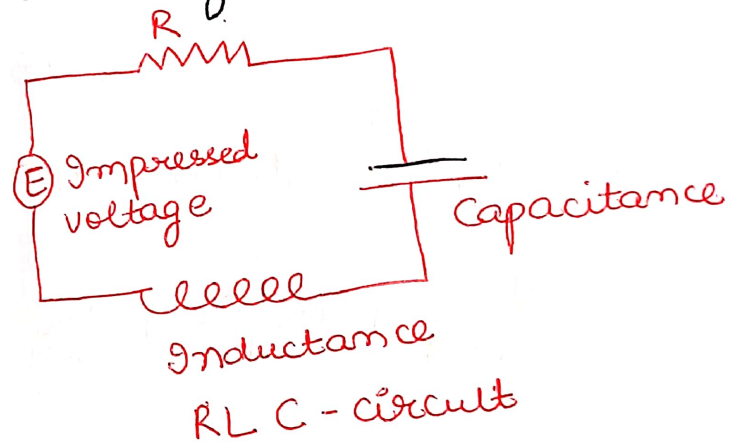

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = E(t) \quad - (2)$$

Differentiate (1) wrt t

$$L \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} I = \frac{dE}{dt}$$

Q A circuit consists of an inductance of 0.05 henrys, a resistance of 5 ohms and a condenser of capacitance 4×10^{-4} farad. If $Q = I = 0$ when $t = 0$ find $Q(t)$ and $I(t)$ when there is a constant emf of 110 volts.

Sol $L = 0.05$, $R = 5$, $C = 4 \times 10^{-4}$, $E = 110$

The differential equation of RLC-circuit

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = E(t)$$

$$0.05 \frac{d^2 Q}{dt^2} + 5 \frac{dQ}{dt} + \frac{Q}{4 \times 10^{-4}} = 110$$

$$\text{or } \frac{d^2 Q}{dt^2} + 100 \frac{dQ}{dt} + 50,000 Q = 2200$$

$$m^2 + 100m + 50,000 = 0$$

$$m = -50 \pm 50\sqrt{19}i$$

$$C_F = e^{-50t} (A \cos 50\sqrt{19}t + B \sin 50\sqrt{19}t)$$

$$Q_p = \frac{1}{D^2 + 100D + 50,000} \quad 2200 = \frac{2200}{50,000} = \frac{11}{2500}$$

$$Q_s = e^{-50t} (A \cos \omega t + B \sin \omega t) + \frac{11}{2500}$$

$$\omega = 50\sqrt{19}$$

$$Q = 0 \quad \text{at } t = 0.$$

$$0 = A + \frac{11}{2500}$$

$$A = -\frac{11}{2500}$$

Differentiating Q w.r.t

$$\frac{dQ}{dt} = e^{-50t} (-\omega A \sin \omega t + B \omega \cos \omega t) - 50 e^{-50t} (A \cos \omega t + B \sin \omega t)$$

Since $I = 0$ at $t = 0$, we have.

$$0 = B\omega - 50A \quad \text{or} \quad B = \frac{50A}{\omega}$$

$$I(t) = e^{-50t} ($$

$$I(t) = \frac{44}{\sqrt{19}} e^{-50t} \sin 50\sqrt{19} t.$$